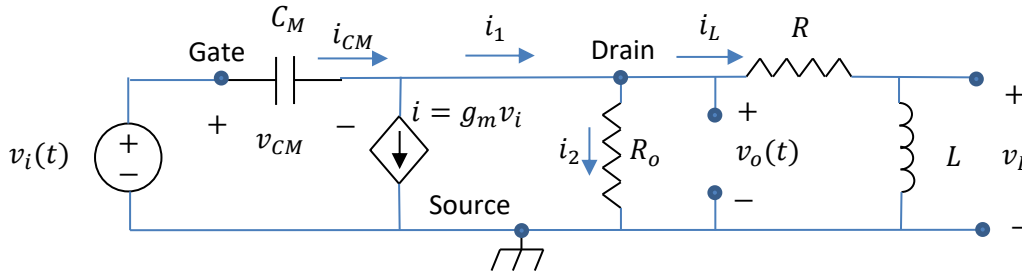


A. A small signal model of an N type MOSFET driving an inductive load is shown below. Use circuit theory to find the system differential equations in the state space matrix form as in eq. (5 – 1) and (5 – 2) in Handout 5. Remember: there is going to be one first order differential equation per storage element (i.e. an inductor or a capacitor).

- What is the order of the system?
- What are the state variables?



List of constants and variables:

- $v_i(t)$  = System input (volts).
- $v_o(t)$  = System output (volts).
- $g_m$  = Transconductance (constant) (S) = ( $\Omega^{-1}$ )
- $C_M = c_{gd}$  = Miller capacitance (constant) (F). It is between input and output and creates an undesirable feedback.
- $R_o$  = Output resistance (constant) ( $\Omega$ ).
- $R$  = Load resistance (constant) ( $\Omega$ ).
- $L$  = Load inductance (constant) (H).

#### ANSWER A:

- First identify the energy storage elements and write their equations:

$$C_M: i_{CM} = C_M \frac{dv_{CM}}{dt}; \quad L: v_L = L \frac{di_L}{dt}$$

- State variables are those whose derivatives exist; hence the state vector is:

$$\mathbf{x} = \begin{bmatrix} v_{CM} \\ i_L \end{bmatrix}$$

- Rewrite energy storage elements equations with derivatives alone on the left hand side:

$$C_M: \frac{dv_{CM}}{dt} = \frac{1}{C_M} i_{CM}; \quad L: \frac{di_L}{dt} = \frac{1}{L} v_L \Rightarrow \frac{d}{dt} \begin{bmatrix} v_{CM} \\ i_L \end{bmatrix} = \begin{bmatrix} \frac{1}{C_M} i_{CM} \\ \frac{1}{L} v_L \end{bmatrix} \quad (1)$$

- Now find the right hand side, i.e.  $i_{CM}$  and  $v_L$ , in terms of state variables  $v_{CM}$ ,  $i_L$  and input  $v_i$  from above circuit.

- To do so, first write the general state space equations (input is  $v_i$ , output is  $v_o$ ):

$$\frac{d\mathbf{x}}{dt} = \frac{d}{dt} \begin{bmatrix} v_{CM} \\ i_L \end{bmatrix} = \mathbf{A} \begin{bmatrix} v_{CM} \\ i_L \end{bmatrix} + \mathbf{B} v_i$$

$$\mathbf{y} = v_o = \mathbf{C} \begin{bmatrix} v_{CM} \\ i_L \end{bmatrix} + \mathbf{D} v_i$$

- Note the dimensions of variables: input size = 1, output size = 1, state vector size = 2; hence:  $\mathbf{A}$  is 2 X 2,  $\mathbf{B}$  is 2 X 1,  $\mathbf{C}$  is 1 X 2 and  $\mathbf{D}$  is 1 X 1; substitute equation 1 for the derivatives:

$$\frac{d}{dt} \begin{bmatrix} v_{CM} \\ i_L \end{bmatrix} = \begin{bmatrix} \frac{1}{C_M} i_{CM} \\ \frac{1}{L} v_L \end{bmatrix} = \overbrace{\begin{bmatrix} \dots & \dots \\ \dots & \dots \end{bmatrix}}^{\mathbf{A}} \begin{bmatrix} v_{CM} \\ i_L \end{bmatrix} + \overbrace{\begin{bmatrix} \dots \\ \dots \end{bmatrix}}^{\mathbf{B}} v_i \quad (2)$$

$$v_o = \overbrace{\begin{bmatrix} \dots & \dots \end{bmatrix}}^{\mathbf{C}} \begin{bmatrix} v_{CM} \\ i_L \end{bmatrix} + \overbrace{\begin{bmatrix} \dots \end{bmatrix}}^{\mathbf{D}} v_i \quad (3)$$

- It is easier to begin with an equation for  $v_o$  as  $v_o$  is used in future; apply Kirchhoff's voltage law (KVL) around the outer loop:

$$v_i = v_{CM} + v_o \Rightarrow v_o = -v_{CM} + v_i \quad (4)$$

- From above, the matrix expression for output  $v_o$  may be written:

$$v_o = \overbrace{\begin{bmatrix} -1 & 0 \end{bmatrix}}^{\mathbf{C}} \begin{bmatrix} v_{CM} \\ i_L \end{bmatrix} + \overbrace{\begin{bmatrix} 1 \end{bmatrix}}^{\mathbf{D}} v_i \quad (5)$$

- To find the first row of  $\mathbf{A}$  and  $\mathbf{B}$  matrices in equation (2), apply Kirchhoff's current law (KCL) at the node right after the capacitor (see figure on page 1):

$$i_{CM} = i + i_1; \quad i = g_m v_i \Rightarrow i_{CM} = g_m v_i + i_1 \quad (6)$$

- Apply KCL at "Drain" node in the figure:

$$i_1 = i_2 + i_L; \quad i_2 = \frac{v_o}{R_o} \Rightarrow i_1 = \frac{v_o}{R_o} + i_L \quad (7)$$

- Substitute for:  $v_o$  from (4):

$$i_1 = \frac{-v_{CM} + v_i}{R_o} + i_L \quad (8)$$

- Substitute (8) in (6):

$$i_{CM} = g_m v_i + i_1 \Rightarrow i_{CM} = g_m v_i + \frac{-v_{CM} + v_i}{R_o} + i_L \quad (9)$$

- Factor  $v_i$  and rewrite (9) in proper variables order:

$$i_{CM} = -\frac{1}{R_o} v_{CM} + i_L + \left(g_m + \frac{1}{R_o}\right) v_i \quad (10)$$

- Divide (10) by  $1/C_M$ :

$$\frac{1}{C_M} i_{CM} = -\frac{1}{R_o C_M} v_{CM} + \frac{1}{C_M} i_L + \left(\frac{g_m}{C_M} + \frac{1}{R_o C_M}\right) v_i \quad (11)$$

- The first row of **A** and **B** matrices in equation (2) may now be filled:

$$\frac{d}{dt} \begin{bmatrix} v_{CM} \\ i_L \end{bmatrix} = \begin{bmatrix} \frac{1}{C_M} i_{CM} \\ \frac{1}{L} v_L \end{bmatrix} = \overbrace{\begin{bmatrix} -\frac{1}{R_o C_M} & \frac{1}{C_M} \\ \dots & \dots \end{bmatrix}}^{\mathbf{A}} \begin{bmatrix} v_{CM} \\ i_L \end{bmatrix} + \overbrace{\begin{bmatrix} \frac{g_m}{C_M} + \frac{1}{R_o C_M} \\ \dots \end{bmatrix}}^{\mathbf{B}} v_i \quad (12)$$

- It remains to find  $v_L$  in terms of  $v_{CM}, i_L, v_i$ . Note that:

$$v_o = i_L R + v_L \Rightarrow v_L = v_o - i_L R \quad (13)$$

- Substitute for  $v_o$  from (4):

$$v_L = v_o - i_L R; v_o = -v_{CM} + v_i \Rightarrow v_L = -v_{CM} + v_i - i_L R \quad (14)$$

- Divide above by  $L$  and rewrite in proper variables order:

$$\frac{1}{L} v_L = -\frac{1}{L} v_{CM} - \frac{R}{L} i_L + \frac{1}{L} v_i \quad (15)$$

- The 2<sup>nd</sup> row of (12) may now be filled:

$$\frac{d}{dt} \begin{bmatrix} v_{CM} \\ i_L \end{bmatrix} = \begin{bmatrix} \frac{1}{C_M} i_{CM} \\ \frac{1}{L} v_L \end{bmatrix} = \overbrace{\begin{bmatrix} -\frac{1}{R_o C_M} & \frac{1}{C_M} \\ -\frac{1}{L} & -\frac{R}{L} \end{bmatrix}}^{\mathbf{A}} \begin{bmatrix} v_{CM} \\ i_L \end{bmatrix} + \overbrace{\begin{bmatrix} \frac{g_m}{C_M} + \frac{1}{R_o C_M} \\ \frac{1}{L} \end{bmatrix}}^{\mathbf{B}} v_i \quad (16)$$

- Final answer:

$$\underbrace{\frac{d}{dt} \begin{bmatrix} v_{CM} \\ i_L \end{bmatrix}}_{\mathbf{dx/dt}} = \overbrace{\begin{bmatrix} -\frac{1}{R_o C_M} & \frac{1}{C_M} \\ -\frac{1}{L} & -\frac{R}{L} \end{bmatrix}}^{\mathbf{A}} \underbrace{\begin{bmatrix} v_{CM} \\ i_L \end{bmatrix}}_{\mathbf{x}} + \overbrace{\begin{bmatrix} \frac{g_m}{C_M} + \frac{1}{R_o C_M} \\ \frac{1}{L} \end{bmatrix}}^{\mathbf{B}} \underbrace{v_i}_{\mathbf{u}} ; \quad \underbrace{v_o}_{\mathbf{y}} = \overbrace{\begin{bmatrix} -1 & 0 \end{bmatrix}}^{\mathbf{C}} \underbrace{\begin{bmatrix} v_{CM} \\ i_L \end{bmatrix}}_{\mathbf{x}} + \overbrace{\begin{bmatrix} 1 \end{bmatrix}}^{\mathbf{D}} \underbrace{v_i}_{\mathbf{u}}$$

B. (Use MATLAB) Substitute the following numbers for the constants in the system state space differential equations and find the system transfer function  $G(s) = \frac{V_o(s)}{V_i(s)}$  by equation (5 – 7) in

Handout 5 (all numbers: 5 significant digits i.e. use “vpa(..., 5)” command:

- $g_m = 0.005$  S.
- $C_M = 20 \times 10^{-12}$  F.
- $R_o = 200$   $\Omega$
- $R = 1000$   $\Omega$
- $L = 10^{-4}$  H

C. When  $v_i$  is a step input of 1 volt, find the system response  $v_o(t)$  by finding the inverse Laplace transform of  $V_o(s)$  symbolically by MATLAB. Plot system response  $v_o$  vs. time using MATLAB control system toolbox: first define the transfer function by “tf” command and then use “step” command to plot the response (don’t specify the final time in step command).

### COMMENTS:

- As seen below, the step response is negative even though the input is a positive unit step; this is because the circuit is an inverting amplifier.
- Compare the symbolic results to that of the control system toolbox. Note that  $y(t)$  obtained symbolically is an exact closed form solution which is not available in control system toolbox.

### PART B:

```
syms s t          % Laplace symbols.

% Circuit Data:
gm = 0.005;
cm = 20e-12;
ro = 200;
r = 1000;
l = 1e-4;

% A,B,C,D matrices:
A = [-1/(cm*ro), 1/cm; -1/l, -r/l]
B = [gm/cm + 1/(ro*cm); 1/l]
C = [-1, 0]
D = 1

Gs = C * (s*eye(2) - A)^-1 * B + D;
Gs = simplifyFraction(Gs);
vpa(Gs, 5);
disp(' ***** G(s): ')
pretty(ans)

% Make the leading coefficient in denominator = 1:

[NN, DD] = numden(Gs) % Separate the numerator and denominator.
DDcs = coeffs(DD) % Find denominator coefficients of powers of s.
DD = DD/DDcs(3) % Divide both denominator and numerator by the
```

```

% coeff of s^2.
NN = NN/DDcs(3)

DD = collect(DD)
NN = collect(NN)

% Reconstruct G(s):
Gs = NN/DD

% Answer part B:

disp(' ***** simplified G(s):')
vpa(Gs, 5)
pretty(ans)
%
```

A =

```

1.0e+10 *

-0.0250    5.0000
-0.0000   -0.0010
```

B =

```

1.0e+08 *

5.0000
0.0001
```

C =

```

-1    0
```

D =

```

1
```

```

***** G(s):
          7 2          15          22
(- 3.3554 10 s + 8.0531 10 s + 8.3886 10 ) 1.0
-----
          7 2          15          23
3.3554 10 s + 8.7242 10 s + 1.0066 10
```

NN =

```

33554432*s^2 - 80530636800000001*s - 83886080000000010000000
```

# Group Assignment 1 Solution

Due Monday Sept. 19

Sept. 13, 2016

ENGR 447-01 Control Systems (Fall 2016)

Page 6 of 7

DD =

$$33554432*s^2 + 8724152320000001*s + 100663296000000010000000$$

DDCs =

$$[ 100663296000000010000000, 8724152320000001, 33554432]$$

DD =

$$s^2 + (8724152320000001*s)/33554432 + 786432000000000078125/262144$$

NN =

$$s^2 - (8053063680000001*s)/33554432 - 655360000000000078125/262144$$

DD =

$$s^2 + (8724152320000001*s)/33554432 + 786432000000000078125/262144$$

NN =

$$s^2 - (8053063680000001*s)/33554432 - 655360000000000078125/262144$$

GS =

$$-(-s^2 + (8053063680000001*s)/33554432 + 655360000000000078125/262144)/(s^2 + (8724152320000001*s)/33554432 + 786432000000000078125/262144)$$

\*\*\*\*\* simplified G(s):

ans =

$$-(1.0*(-1.0*s^2 + 2.4e8*s + 2.5e15))/(s^2 + 2.6e8*s + 3.0e15)$$

$$\frac{(-1.0s^2 + 2.4 \cdot 10^8 s + 2.5 \cdot 10^{15}) \cdot 1.0}{s^2 + 2.6 \cdot 10^8 s + 3.0 \cdot 10^{15}}$$

Part C:

```
Ys = Gs * 1/s
Ys = vpa(Ys,5);
yt = ilaplace(Ys);
```

```
% Answer C:
```

```
yt = vpa(yt,5)
```

```
% Plotting using control system toolbox ss, tf and step commands:
```

```
Gss = ss(A,B,C,D); % Define state space system.
```

```
Gs = tf(Gss) % Find its transfer function.
```

```
step(Gs) % Plot step response.
```

```
Ys =
```

```
-(- s^2 + (8053063680000001*s)/33554432 + 65536000000000078125/262144)/(s*(s^2 +  
(8724152320000001*s)/33554432 + 78643200000000078125/262144))
```

```
yt =
```

```
2.0264*exp(-2.479e8*t) - 0.19305*exp(-1.2102e7*t) - 0.83333
```

```
Gs =
```

$$\frac{s^2 - 2.4e08 s - 2.5e15}{s^2 + 2.6e08 s + 3e15}$$

```
Continuous-time transfer function.
```

